



M 8855

Reg. No. :

Name :

II Semester B.C.A. Degree (CCSS – 2014 Admn. – Regular)

Examination, May 2015

CORE COURSE

2B02 BCA : Digital Systems

Time : 3 Hours

Max. Marks : 40

SECTION – A

1. **One word answer :**

(8×0.5=4)

- a) In digital computer, _____ is used to represent negative numbers.
- b) The output of a NOR gate is high if all inputs are _____.
- c) An octal digit corresponds to _____ binary digits.
- d) A BCD counter has _____ states.
- e) The number of control lines for a 8 to 1 multiplexer is _____.
- f) The Gray code for decimal number 6 is equivalent to _____.
- g) The device which changes from serial data to parallel data is _____.
- h) The excess 3 code of decimal number 26 is _____.

SECTION – B

Write short notes on **any seven** of the following questions.

(7×2=14)

2. State and prove commutative law of Boolean algebra.
3. Describe X-OR gate with logic diagram and truth table.
4. Simplify the expression $xyz + xyz' + x'z$.
5. What are synchronous counters ?
6. Convert (110101.101010) to octal and hexadecimal.
7. Define a half adder and full adder.

P.T.O.



8. What is a shift register ? Can a shift register be used as a counter ?
9. What is a demultiplexer ? Discuss the differences between a demultiplexer and a decoder.
10. What is meant by triggering of flip flop ?
11. Explain excess-3 code with examples.

SECTION - C

Answer **any four** of the following questions.

(4×3=12)

12. Simplify the Boolean expression $xy + x'z + yz$.
13. Distinguish between minterms and maxterms.
14. State and prove Demorgan's laws.
15. Implement a full adder circuit with a decoder and two OR gates.
16. What is a flip-flop ? What is the difference between a latch and a flip-flop ? List out the application of flip-flop.
17. Explain the following conversions with suitable examples :
 - a) Decimal to octal
 - b) Octal to hexadecimal.

SECTION - D

Write an essay on **any two** of the following questions.

(2×5=10)

18. What are universal gates ? Construct a logic circuit using NAND gates only for the expression $x = A \cdot (B + C)$.
19. Simplify using K Map in SOP form. $f(A, B, C, D) = \sum(0, 2, 8, 9, 10, 11, 14, 15)$.
20. Explain the working of SR flip-flops.
21. Explain with necessary diagram a Mod - 10 Shift Counter with encoding.